
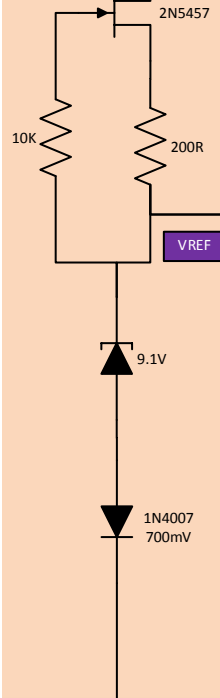



AC → DC + Smoothing

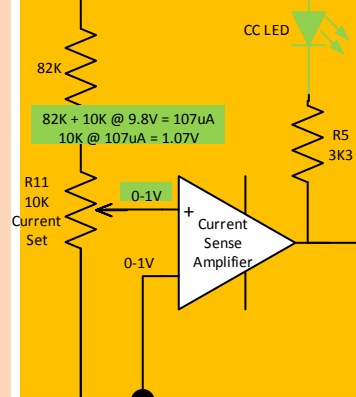


(9.8V) Voltage Reference



Current Control Circuit

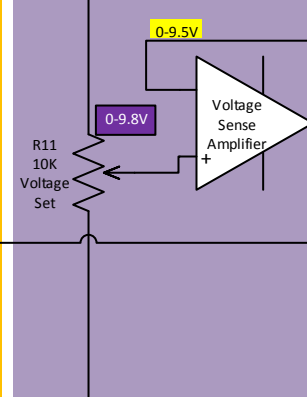

Voltage Control Circuit

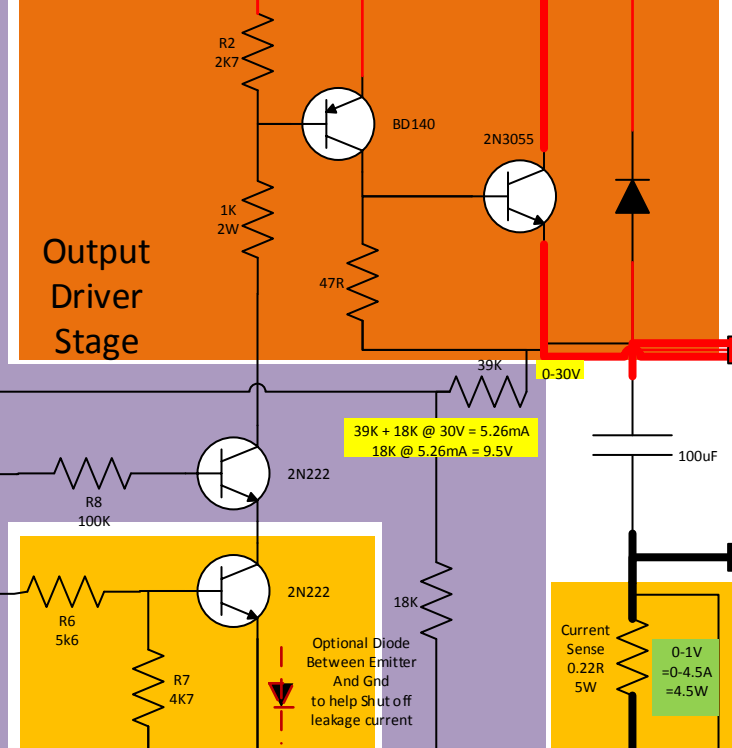

Current Sense 0.22R 5W

+30V DC

0V (GND)

Voltage Reference
Any Voltage will do
As long as it is stable over
time and temperature
Assume 5V

(5V) Voltage
Reference


In this configuration the OP Amp will
do what ever it can to keep the
negative input the same as the
positive input.
Ideal OP Amp is infinite gain and input
input impedance
This means that the negative input will
follow the positive input (0 – 5V) if it
can and within the limits of the supply
and divider network

Voltage Control
Circuit

Output
Driver
Stage

R11
10K
Voltage
Set

0 – 5V
Range

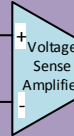

R8
100K

2N222

100K

20K

Divider Network

If you need 0 – 5V to represent 0 – 30V then you need a 5:1 ratio of the resistors
(30V:5V) so maybe 100K and 20K
So when 30V is on output, 5V is presented to OP Amp. If your ratio is slightly off
then error on the side you want.
Remember there will always be a drop across the transistors too so you will never
get the raw supply voltage

R2
2K7


1K
2W


47R

BD140
2N3055


100uF

Output

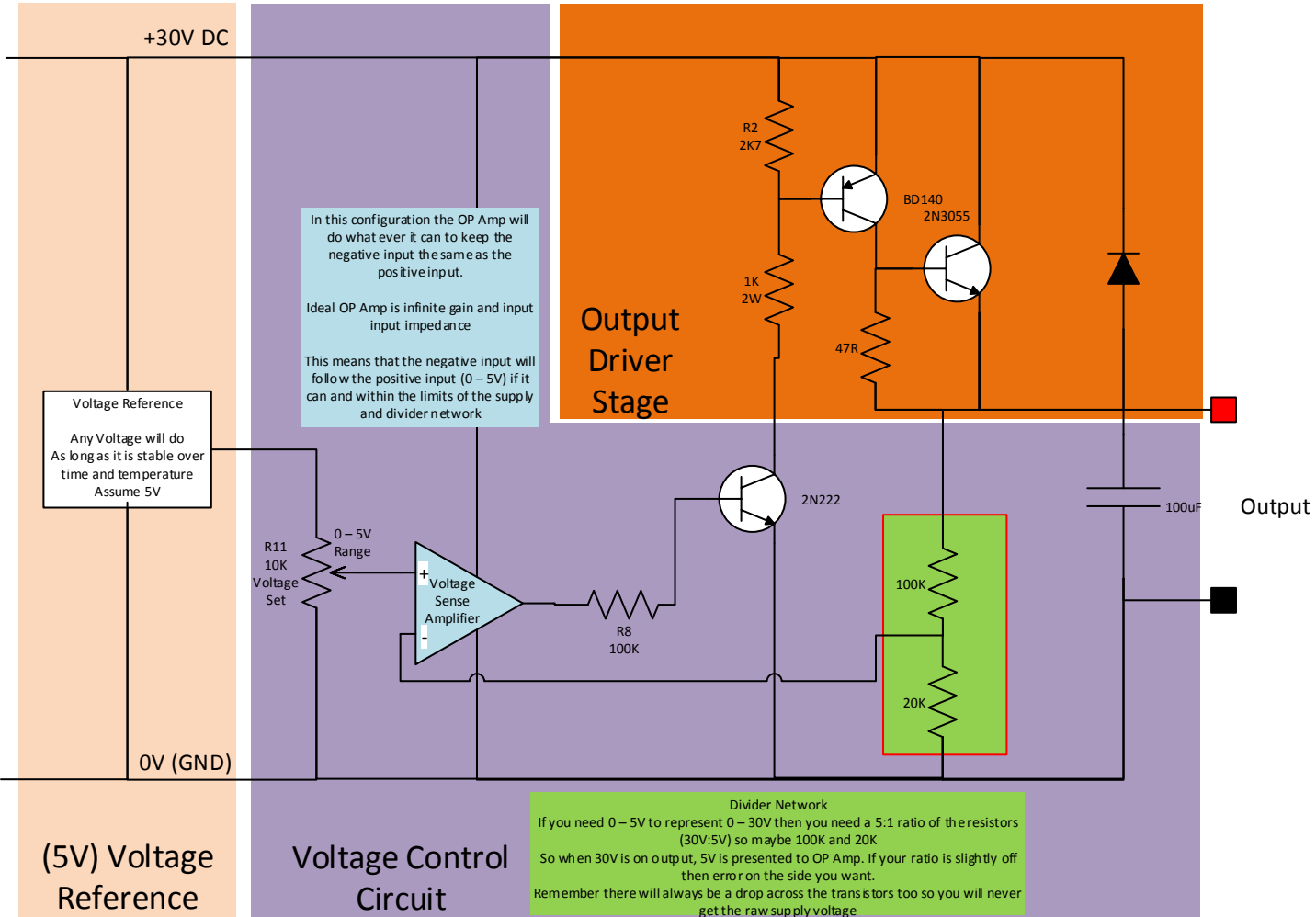


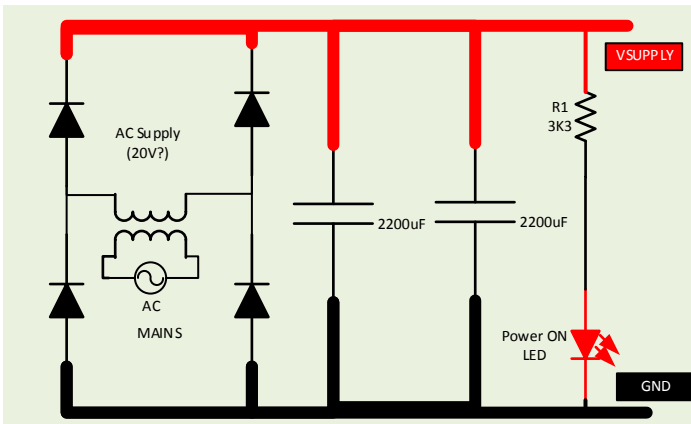


MAIN POWER:- AC Mains to DC

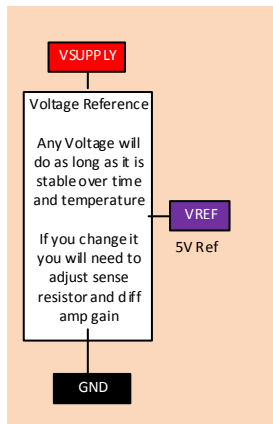


Voltage Reference

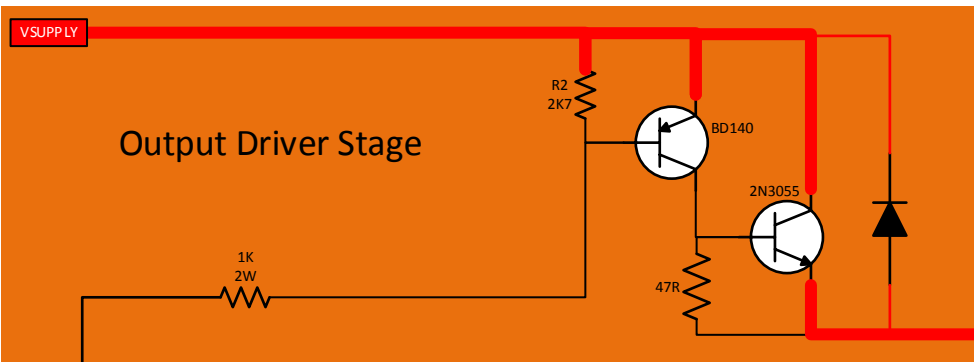


Output Driver Stage

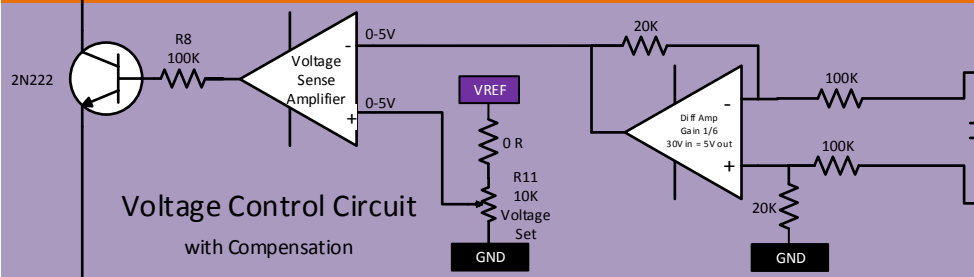

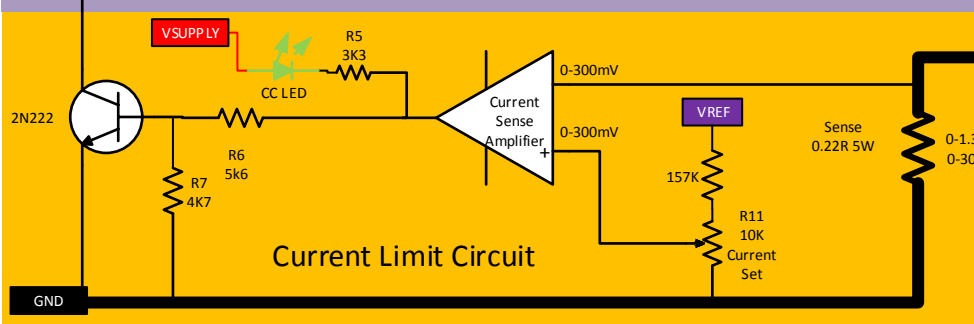
Voltage Control Circuit with Compensation



Current Limit Circuit

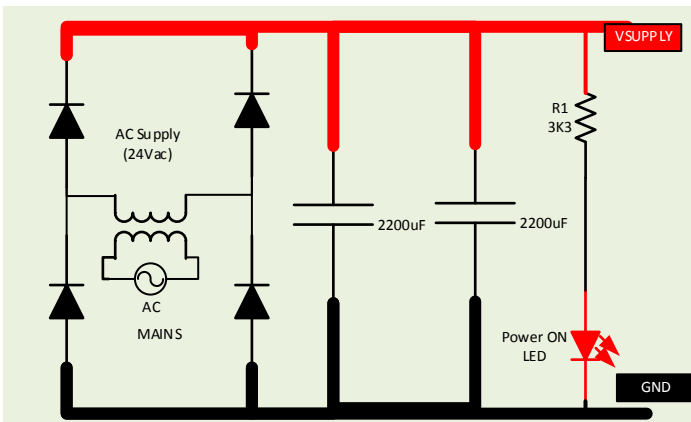

MAIN POWER:- AC Mains to DC

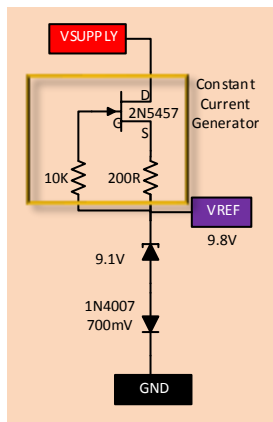

Voltage Reference

